


# ECE 109L - SERIES AND PARALLEL CIRCUITS - LAB 11 EQUIVALENT RESISTANCES

FALL 2006

A.P. FELZER

## OBJECTIVE

The objective of this lab is to calculate and measure equivalent resistances of series and parallel resistor circuits like the following

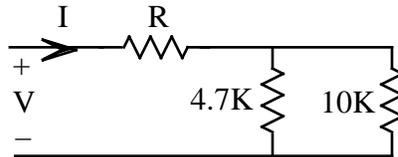


PARTNER 1:  $R = 1K$     PARTNER 2:  $R = 2K$

## LAB

1. Our objective in this first problem is to verify that  $V$  is proportional to  $I$  for the above circuit and then use the result to find  $R_{EQ}$ 
  - a. Measure your resistor values. Compare with the nominal values
  - b. Experimentally determine how  $V$  (in volts) is related to  $I$  (in amps) for the circuit above using the same method as in Lab 5 where we found the resistances of single resistors as follows

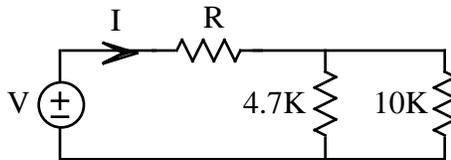
- (1) Connect up a voltage source as follows



- (2) Measure  $I$  (in amps) for "a bunch" of positive as well as negative values of  $V$  (in volts)
  - (3) Plot your data points on a graph of  $V$  as a function of  $I$  and draw the "best fit" line through them. Make sure that your line for  $V$  as a function of  $I$  goes through the origin since resistor circuits cannot have any current flowing through them if the voltage across them is zero
  - (4) Find the slope of your line equal to the equivalent resistance  $R_{EQ} = V/I$  of the resistor circuit
  - (5) And finally make use of your slope to obtain an equation for  $V$  (in **volts**) as a function  $I$  (in **amps**)
- c. Use an ohmmeter to measure  $R_{EQ}$  for your circuit
  - d. Compare your results for  $R_{EQ}$  in parts (b) and (c)
  - e. Now make use of your  $R_{EQ}$  from part (c) to predict  $I$  for when  $V = 2.5$  volts. Be sure to redraw the circuit with the original resistors replaced by  $R_{EQ}$
  - f. Then measure  $I$  when  $V = 2.5$  volts
  - g. Compare your measured and calculated values for  $I$  in parts (e) and (f)


- h. Why do we only need one data point - as measured by an ohmmeter - to determine  $R_{EQ}$  of a resistor circuit

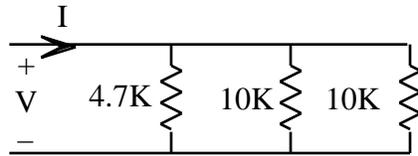2. Given the following parallel resistor circuit




- Measure your resistor values. Compare with nominal values
- Use an ohmmeter to measure  $R_{EQ}$
- Calculate  $R_{EQ}$  by analyzing the circuit with your measured resistor values
- Compare your measured value for  $R_{EQ}$  in part (b) with your calculated value in part (c)

3. Given the following circuit

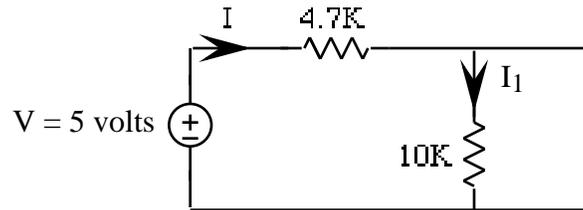

- Measure  $I_1$
- Explain why  $I_1$  has the value it does
- Analyze the circuit to calculate  $R_{EQ} = V/I$
- Measure  $R_{EQ}$  with an ohmmeter
- Compare your calculated and measured values of  $R_{EQ}$

4. Given the following circuit

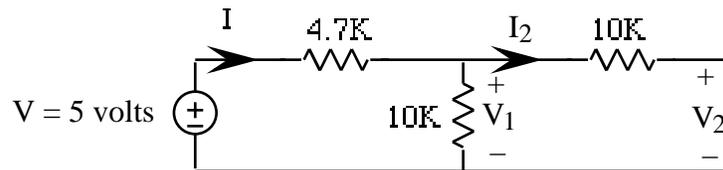

- Measure  $I_2$ ,  $V_1$  and  $V_2$
- Explain why  $I_2$ ,  $V_1$  and  $V_2$  have the values they do
- Analyze the circuit to calculate  $R_{EQ} = V/I$
- Measure  $R_{EQ}$  with an ohmmeter
- Compare your calculated and measured values of  $R_{EQ}$