

# ECE 109L - THE VERY BASICS - LAB 7

## KIRCHHOFF'S CURRENT LAW

FALL 2006

A.P. FELZER


### OBJECTIVE

The objective of this lab is to verify Kirchhoff's Current Law for some simple resistor circuits.


### LAB

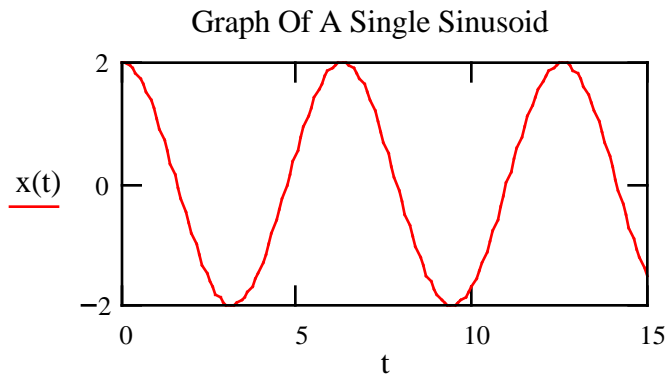1. **Prelab** - First open the Graphing Palette by double clicking on the corresponding icon in the Math Palette. Then run and make a copy of the following Mathcad program for graphing a function.

```
t := 0, 0.1 . . 15  
x(t) := 2*cos (t + 1.2)
```




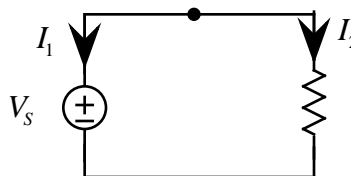1. To obtain the graph of  $x(t)$ 
    - a. Click on the x-y plot icon in the Graphing Palette
    - b. Use the tab to move from one location to another as you type the parameters  $x(t)$ ,  $t$ , . . .
    - c. Click anywhere outside the frame of the graph
    - d. You can now go in and change the values over which  $t$  and  $x(t)$  are plotted
  2. Resize a graph by first selecting it and then holding down the mouse button as you drag along one of the highlighted dots
  3. Change the *format* of a graph by first double clicking on it. You can then change its color, choose solid or dashed lines and so on. You can also change the title by clicking on *labels*
2. From Lab 5 we know that the currents in simple resistor circuits like the following




satisfy  $I_1 = -I_2$  and so add up to zero with  $I_1 + I_2 = 0$ . The objective of this lab is to demonstrate that the sums of currents "leaving" nodes always add up to zero

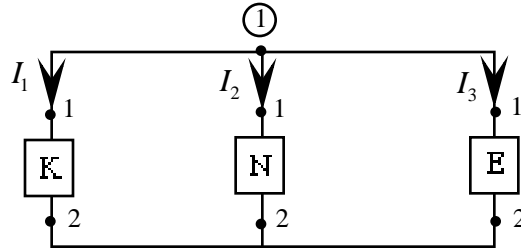Put together the following circuit on your resistor box



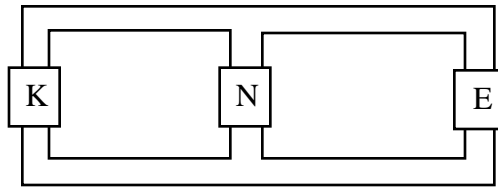- PreLab** - Redraw the circuit with current meters inserted for measuring  $I_1$ ,  $I_2$  and  $I_3$  and with the numbers 1 and 2 showing how the circuit is connected together
- Measure the currents  $I_1$ ,  $I_2$  and  $I_3$
- Now redraw the circuit as follows



and make use of your results in part (b) to indicate which way the equivalent positive charges are flowing through each of the wires

- Find the rate at which equivalent positive charges are entering node 1 in coulombs/sec
  - Find the rate at which equivalent positive charges are leaving node 1 in coulombs/sec
  - What do your results in parts (d) and (e) imply about the rates charges are entering and leaving node 1
3. Verify Kirchhoff's Current Law for the following circuit - that the *algebraic sum* of the currents adds up to zero. As always be sure to draw the circuit, record your measured values and draw a conclusion from your results.

