

ECE 109 - NODE ANALYSIS - INVESTIGATION 16 PRACTICE WITH NODE EQUATIONS

FALL 2006

A.P. FELZER


To do "well" on this investigation you must not only get the right answers but must also do neat, complete and concise writeups that make obvious what each problem is, how you're solving the problem and what your answer is. You also need to include drawings of all circuits as well as appropriate graphs and tables.

We have from the previous investigation the following scheme for analyzing resistor circuits -

- (1) Write and solve the node equations for the node voltages
- (2) Make use of the node voltages to calculate the voltages across and the currents through the resistors
- (3) Make use of the resistor currents to calculate the currents through the voltage sources


The objective of this Investigation is to get some practice writing and solving node equations. As you can imagine, it's very important to keep your equations carefully organized. *So from this point on and forever after you must label every node equation with the node that it's for and put your node equations in matrix form.* Be sure to take a look at the **Computer Demos** on Node Equations.

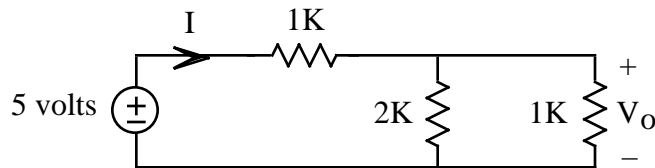1. Make use of node equations to find V_O in the following circuit




And then make use of your result for V_O to calculate I

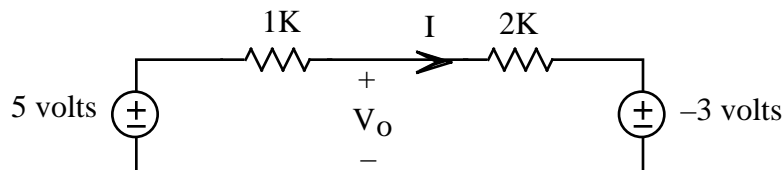2. Make use of node equations to find V_O in the following circuit and then make use of your result for V_O to find I




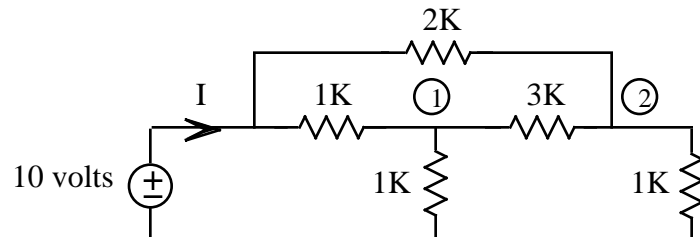3. Make use of node equations to find V_1 and V_2 in the following circuit




and then make use of your results for V_1 and V_2 to calculate I

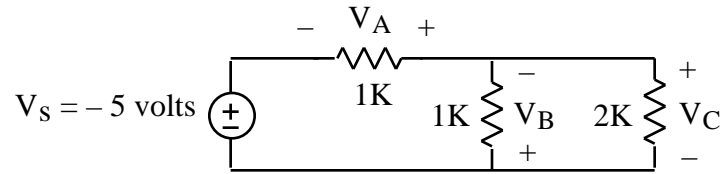
4. Make use of node equations to find V_A , V_B and V_C in the following circuit



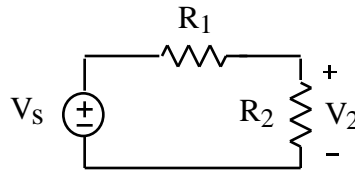
5. Make use of node equations to find the *voltage division equation* for V_2 in the following series circuit



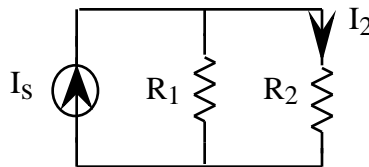6. Make use of node equations to find the *current division equation* for I_2 in the following parallel circuit




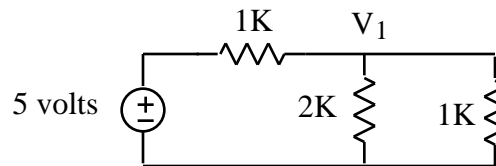7. Make use of node equations to find V_1 in the following circuit




and then make use of your result to find the power for the 2K resistor

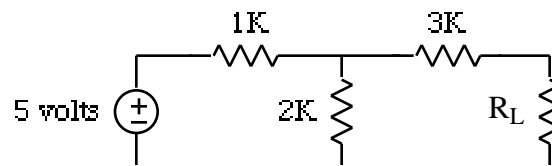
8. The **open circuit voltage drop** at the output of a circuit like the following



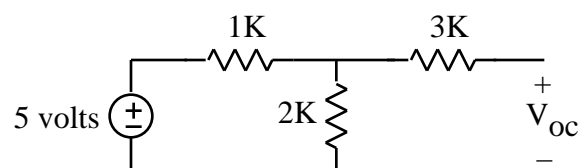is by **definition** the voltage drop V_{oc} when the load R_L is removed as follows




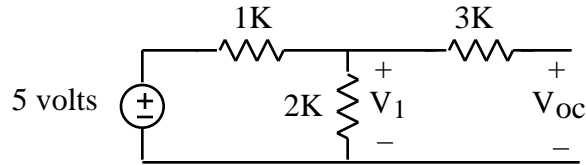- a. Why do you think we call an open circuit voltage drop an open circuit voltage drop
- b. Explain why V_{OC} in our circuit is equal to the voltage drop V_1 across the 2K resistor as follows




- c. Make use of node equations to find V_{OC}


9. Given the following circuit

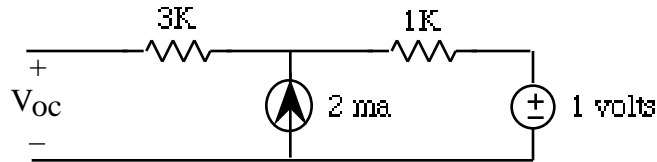

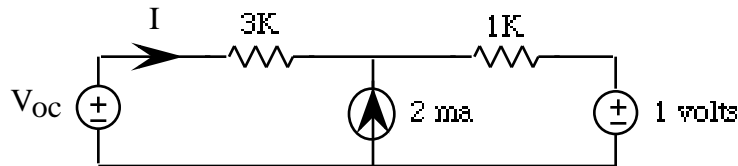- a. Make use of node equations to find the open circuit voltage V_{OC}
- b. Now make use of node equations to find I in the following circuit with V_{OC} equal to the open circuit voltage found in part (a)




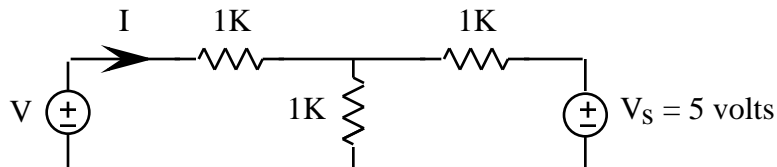10. Generalizing on the result of Problem (9) it can be shown that if $I = 0$ in a circuit as follows




then $V = V_{OC}$. **Memorize** this result. Then confirm it for this circuit.

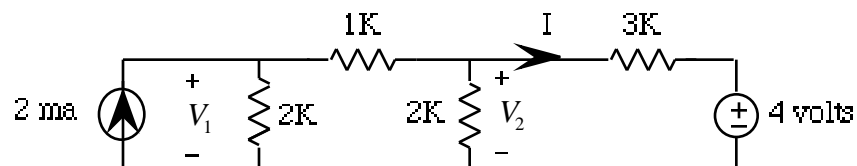11. Use node equations to find V_1 and V_2 in the following circuit




and then make use of your results to calculate I

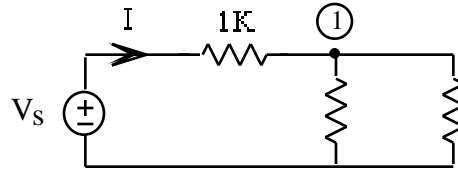12. Find I as a function of V_S in the following circuit if $V_1 = 0.7 V_S$




13. Given the following circuit

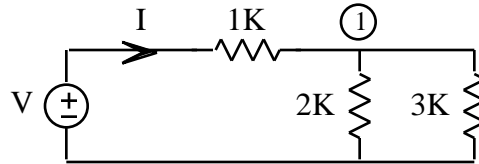


- a. First make use of node equations to find V_1 as a function of V
- b. Then make use of your result in part (a) to find I as a function of V

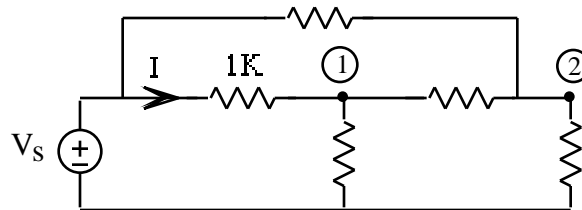14. Explain how you would make use of node analysis to find I as a function of V_s in the following circuit



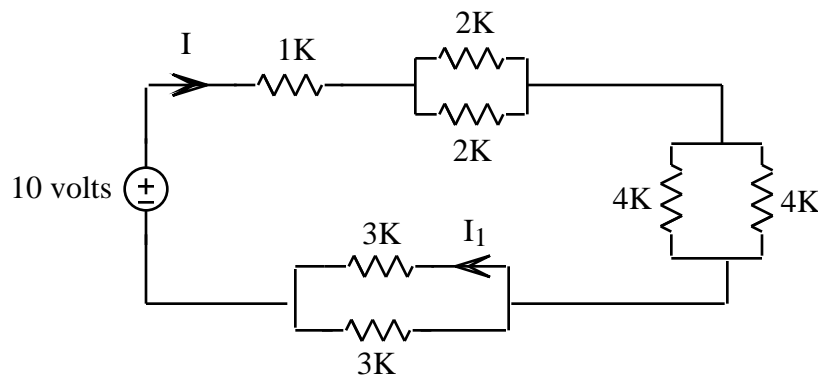15. Find I and I_1 in the following circuit. But beware - node equations are not always the best.



16. Math Review - Given the two points in the xy -plane

- a. Sketch both points in the plane
- b. Find the distance between P_1 and P_2