

ECE 204L - COMBINATIONAL BUILDING BLOCKS - LAB 14 MULTIPLEXERS AND TRI-STATE OUTPUTS

WINTER 2004


A.P. FELZER

OBJECTIVE



The objective of this lab is to show how both multiplexers and tri-state outputs enable signals to share buses.

LAB

1. Given a 2-input, 1-bit MUX as follows

 

  - a. **Prelab** - Explain in words what this MUX is doing
 - b. **Prelab** - Write out the truth table for the MUX
 - c. **Prelab** - Design the circuit with AOI gates
 - d. Build and test your circuit
2. Given the following tri-state buffer
- a. **Prelab** - Write out the truth table for this tri-state buffer
 - a. **Prelab** - Explain in words what this tri-state does
3. **Prelab** - Draw a chip diagram of a 74126 tri-state buffer
 4. Given two tri-state buffers connected to a bus B as follows



- a. **Prelab** - Write out a truth table for the above circuit. Note that $E_0=E_1=1$ are not allowed because we want only one signal to be on the bus at any given time
- b. Test and document the operation of the circuit for each set of allowable inputs. Note that

- the output B at any given time can be 1, 0 or open
- c. Make use of your measured results to complete the following timing diagram

