

ECE 204L - FLIP-FLOPS AND LATCHES - LAB 18

INTRODUCTION TO FLIP-FLOPS

WINTER 2004


A.P. FELZER

OBJECTIVE


The objective of this lab is to build and test master-slave edge-triggered D flip-flops.

LAB

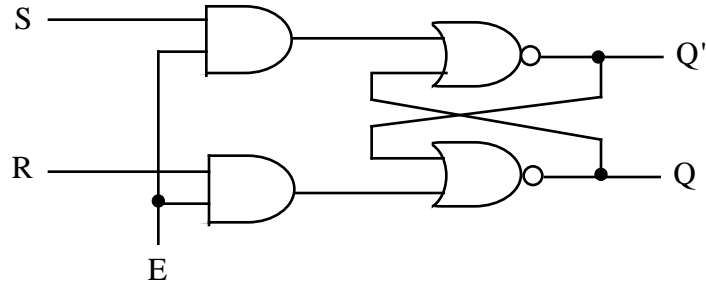
1. Given the following SR latch with enable signal E



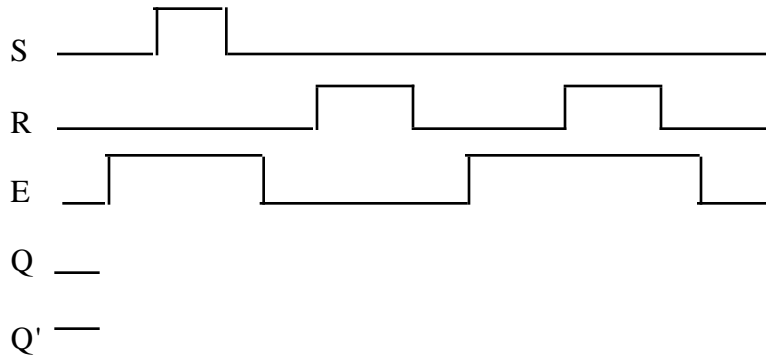
- a. Build and test your circuit. Carefully document your results. Use a DIP switch for S, R and E. As before be sure to put E on the left in your truth table
- b. Make use of your measured results in part (a) to complete the following timing diagram



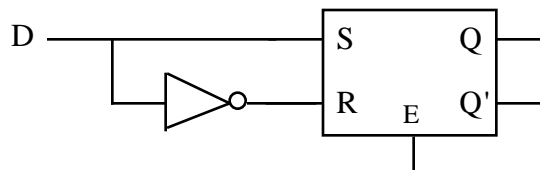
2. Given the following D latch made from the SR latch of Problem (1)



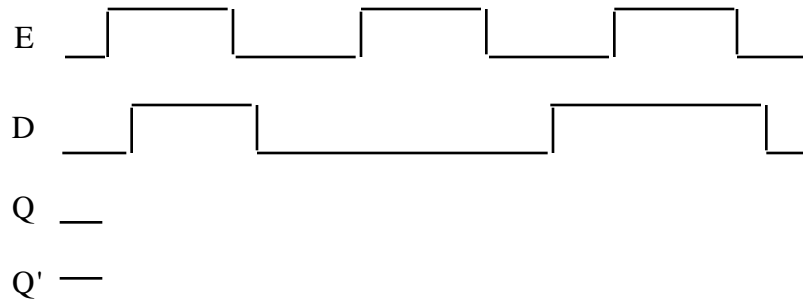- a. Build and test your circuit. Carefully document your results. Use a DIP switch for D and E
- b. Make use of your measured results in part (a) to complete the following timing diagram



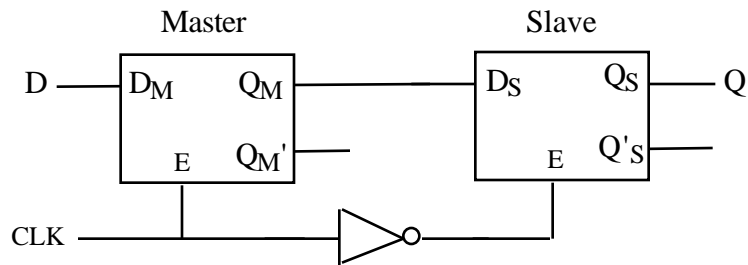3. Given the following master-slave edge-triggered D flip-flop made from D latches of Problem (2) as follows



- a. Build and test your circuit. Carefully document your results. Use LED's at D, Q_M and Q
 b. Make use of your measured results in part (a) to complete the following timing diagram

