

# ECE 204L - COUNTERS - LAB 21 ANALYSIS OF SYNCHRONOUS COUNTERS

WINTER 2004


A.P. FELZER

## OBJECTIVE

The objective of this lab is to build and test a synchronous counter.


## LAB

 1. Verify that a general T flip-flop can be realized with a D flip-flop as follows



by showing that it has the same next state equation

 2. Given the following 3-bit synchronous counter



- a. Draw a logic diagram with pin numbers for this circuit with the T flip-flops implemented with D flip-flops
- b. Calculate the counter's next state table.
- c. Make use of your result in part (b) to draw the counter's state diagram
- d. Build the circuit and then take measurements to obtain the circuit's next state table. Make use of preset and clear to start the counter at zero with  $X_2X_1X_0 = 000$ . Make use of your 7-segment display to display the results
- e. Make use of your measurements in part (d) to draw the counter's state diagram
- f. Compare your measured and calculated results
- g. Make use of your measured results to obtain the circuit's timing diagram starting from the state  $Q_2=Q_1=Q_0=0$
- h. Why do we call this counter a synchronous counter
- i. What happens after 8 clock pulses
- j. Is this an up-counter or a down-counter. How can you tell