

ECE 207L - FIRST ORDER RC CIRCUITS - LAB 13

TIME DELAY OF LOGIC INVERTERS

FALL 2003


A.P. FELZER

OBJECTIVE


The objective of this lab is to illustrate how the pull-up and pull-down resistors R_N and R_P of a CMOS gate can be approximated.

LAB

 1. If we connect a known capacitor C to a CMOS inverter as follows



with equivalent circuit as follows

 

then we should be able to calculate R_N and R_P by measuring the time constants τ_{pu} and τ_{pd} for pull-up and pull-down when the input $v_s(t)$ is a pulse train. Do this for your inverter as if it was a CMOS inverter. Note that you'll have to keep increasing the frequency of the input pulse train until you get a good display of the transient response