

ECE 207L - FIRST ORDER RC CIRCUITS - LAB 16 INTERCONNECTS IN CMOS INTEGRATED CIRCUITS

FALL 2003


A.P. FELZER

OBJECTIVE

The objective of this lab is to model the affects of the interconnects in CMOS integrated circuits with two lump RC circuits.

LAB

1. Given the following two lump RC circuit for modeling interconnects in CMOS integrated circuits

 

PARTNER 1: $R = 1K$ PARTNER 2: $R = 2K$

- a. Measure your resistor and capacitor values. Compare with nominal values
- b. Sketch what you expect for $v_{C2}(t)$ during pull-up assuming the voltages across the capacitors start from 0 volts. What is the final steady state value
- c. Sketch what you expect for $v_{C2}(t)$ during pull-down assuming the voltages across the capacitors are initially 5 volts
- d. Now connect up your circuit to the scope and make use of what you see to sketch $v_{C2}(t)$ during pull-up and during pull-down. How do your sketches compare to what you expected in parts (b) and (c)
- e. Measure the time it takes $v_{C2}(t)$ to increase from 0 volts to 4 volts during pull-up and the time it takes $v_{C2}(t)$ to decrease from 5 volts to 1 volt during pull-down
- f. Do the analysis to come up with equations for $v_{C2}(t)$ during pull-up and pull-down.
- g. Make use of Mathcad to plot your equations in part (f)
- h. Make use of your graphs in part (g) to find the time it takes $v_{C2}(t)$ to increase from 0 volts to 4 volts during pull-up and the time it takes $v_{C2}(t)$ to decrease from 5 volts to 1 volt during pull-down
- i. Compare your calculated and measured results in parts (e) and (h)