

ECE 207L - FIRST ORDER RL CIRCUITS - LAB 18

INTRODUCTION TO INDUCTORS

FALL 2003

A.P. FELZER


OBJECTIVE

The objective of this lab is to demonstrate that an inductor's voltage $v_L(t)$ and current $i_L(t)$ are related as follows

$$v_L(t) = L \frac{di_L(t)}{dt}$$

LAB

1. Given the following circuit

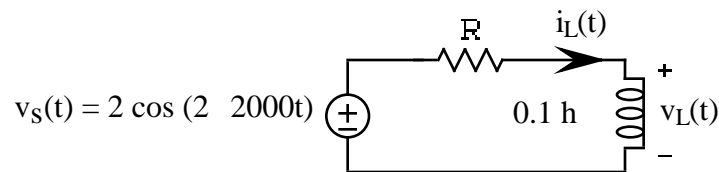

PARTNER 1: $R = 1K$ PARTNER 2: $R = 2K$

- Measure your resistor and inductor values. Compare with nominal values
- Measure the amplitudes and phases of $i_L(t)$ and $v_L(t)$. The phases should be with respect to $v_s(t)$.
- Make use your results in part (b) to write expressions for $i_L(t)$ and $v_L(t)$ as cosines
- Make use of your measured value for $i_L(t)$ to calculate $v_L(t)$ from the expression

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Express your result as a cosine.

- Compare your calculated and measured values in parts (b) and (d) for the amplitude and phase of $v_L(t)$
2. Given any two inductors L_1 and L_2
- Measure their values
 - Calculate the equivalent inductances when they're connected in series and when they're connected in parallel
 - Measure the equivalent inductances when they're connected in series and when they're connected in parallel
 - Now compare you measured and calculated equivalent inductances in parts (b) and (c)