

ECE 207L - FIRST ORDER RC CIRCUITS - LAB 9

INTRODUCTION TO CAPACITORS

FALL 2003

A.P. FELZER


OBJECTIVE

The objective of this lab is to demonstrate that a capacitor's current $i_C(t)$ and voltage $v_C(t)$ are related as follows

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

LAB

1. Given the following circuit

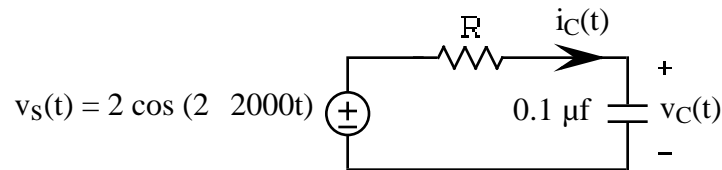

PARTNER 1: $R = 1\text{K}$ PARTNER 2: $R = 2\text{K}$

- Measure your resistor and capacitor values. Compare with nominal values
- Measure the amplitudes and phases of $i_C(t)$ and $v_C(t)$. The phases should be with respect to $v_S(t)$. Show your calculations along with corresponding graphs.
- Make use of your results in part (b) to write expressions for $i_C(t)$ and $v_C(t)$ as cosines with positive coefficients. What is the phase difference between your $i_C(t)$ and $v_C(t)$
- Make use of your measured value for $v_C(t)$ to calculate $i_C(t)$ from the expression

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Express your result as a cosine. What is the phase difference between your $i_C(t)$ and $v_C(t)$

- Compare your calculated and measured values in parts (b) and (d) for the amplitude of $i_C(t)$ and the phase difference between your $i_C(t)$ and $v_C(t)$
2. Given any two capacitors C_1 and C_2
- Measure their values
 - Measure the equivalent capacitances when they're connected in series and when they're connected in parallel
 - Calculate the equivalent capacitances when they're connected in series and when they're connected in parallel
 - Compare your measured and calculated equivalent capacitances in parts (b) and (c)