


ECE 209 - SECOND ORDER CIRCUITS - INV 10 FREQUENCY RESPONSES OF SERIES RLC CIRCUITS

FALL 2000


A.P. FELZER

To do "well" on this investigation you must not only get the right answers but must also do neat, complete and concise writeups that make obvious what each problem is, how you're solving the problem and what your answer is. You also need to include drawings of all circuits as well as appropriate graphs and tables.

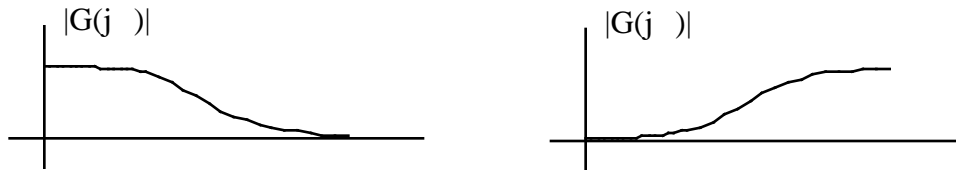
Up to now we've been studying first order RC and RL circuits with lowpass and highpass frequency responses like the following



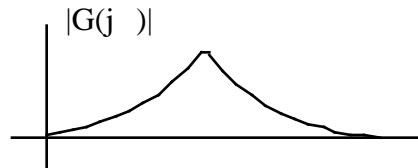
These circuits are great for many applications but to obtain a circuit with a bandpass response like this



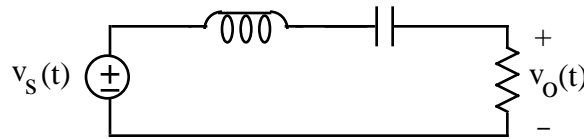we need to build 2nd order circuits like the following second order series RLC circuit



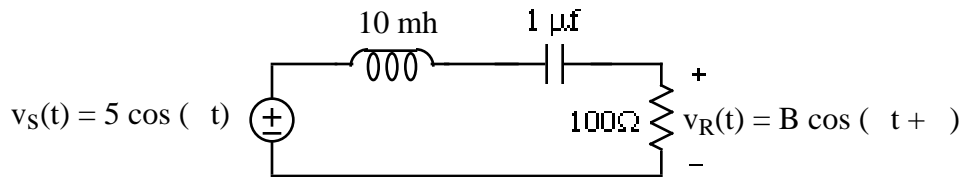1. Describe how the frequency responses of bandpass circuits are different from those of lowpass and highpass circuits.
2. The objective of this problem is to see how the amplitude B of the sinusoidal steady state response of $v_R(t)$ in the following series RLC circuit




varies as a function of frequency ω .

- a. Find the steady state response of $v_R(t)$ when the input is a constant - a sinusoid of frequency $\omega = 0$.
- b. What would you expect happens to the amplitude of $v_R(t)$ as ω increases from 0. Test your result by calculating B at $\omega = 500$ rad/sec

- c. Find the steady state response of $v_R(t)$ when $\omega = 1000$.
- d. Make use of your results in parts (a)-(c) to sketch $|V_R(j\omega)|$ as a function of frequency ω . Note that we refer to second order bandpass circuits like the one we've been analyzing in this problem as **resonant** circuits.

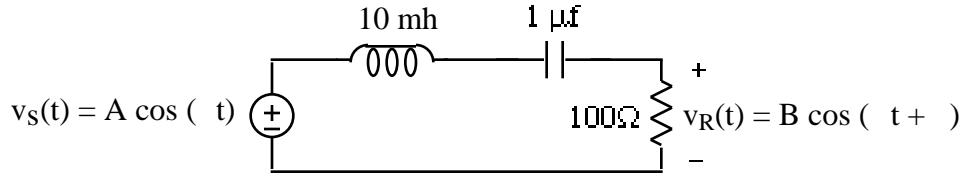3. The objective of this problem is to calculate and sketch the transfer function



of the bandpass circuit in Problem (2) as given by


$$G(j\omega) = \frac{V_R(j\omega)}{V_s}$$

- a. Find $G(j\omega) = V_R(j\omega)/V_s$
 - b. Use Mathcad to obtain a graph of $|G(j\omega)|$ as a function of ω on a log scale
 - c. Describe your graph in part (b)
 - d. Reconcile any differences between your graphs in part (b) of this problem and part (d) in Problem (2)
4. Find the sinusoidal steady state response of a second order series RLC circuit with the following transfer function

$$G(j\omega) = \frac{V_R(j\omega)}{V_s} = \frac{1000(j\omega)}{(j\omega)^2 + 1000(j\omega) + 10^6}$$


to the input $v_s(t) = 5 \cos(1000t)$

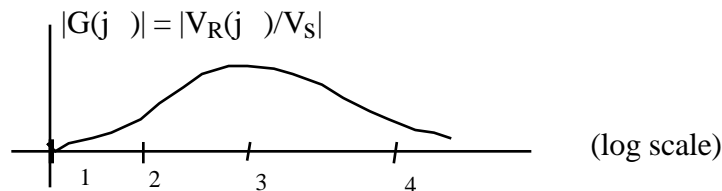5. The objective of this problem is to sketch graphs of what we would see on a scope as we increase the frequency in a series RLC resonant circuit like the one in Problems (2) and (3) with frequency responses as follows



- a. Sketch $v_s(t)$ and the sinusoidal steady state response $v_R(t)$ at each of the frequencies $\omega = 1, 2, 3, 4$. Put all sketches on separate graphs.
 - b. Describe what's happening to the steady state response of $v_R(t)$ as ω increases from 0
6. The objective of this problem is to define what we mean by the resonance frequency ω_p and what we mean by the 3dB bandwidth of a bandpass circuit. Given the following series RLC


circuit

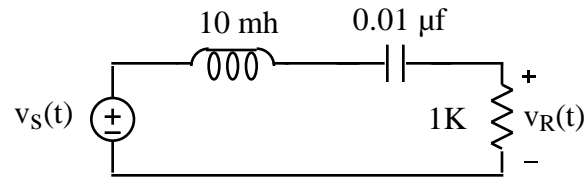

with bandpass transfer function as follows

$$G(j\omega) = \frac{V_R(j\omega)}{V_s} = \frac{10^5(j\omega)}{(j\omega)^2 + 10^5(j\omega) + 10^{10}}$$

- Use Mathcad to obtain a graph of $|G(j\omega)| = |V_R(j\omega)/V_s|$ versus ω on a log scale.
 - Make use of your graph in part (a) to find the **resonance frequency** ω_p - the frequency where the response is maximum. Note that a resonant circuit is said to be in **resonance** at the frequency ω_p
 - Make use of your graph in part (a) to find the lower and upper 3dB frequencies $\omega_{\ell 3dB}$ and $\omega_{u 3dB}$ of $G(j\omega)$
 - Make use of your result in part (c) to find the **3dB Bandwidth** as defined by $3dB BW = \omega_{u 3dB} - \omega_{\ell 3dB}$
7. The objective of this problem is to analyze a general 2nd order series RLC resonant circuit as given by

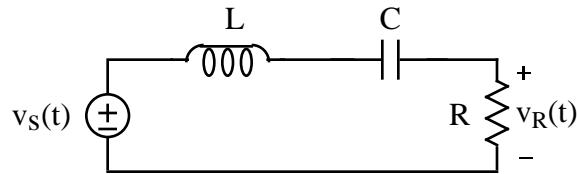

- Verify that the voltage transfer function is


$$G(j\omega) = \frac{V_R(j\omega)}{V_s} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j\omega L - \frac{1}{\omega C}}$$

- Use your result in part (a) to obtain a general expression for the resonant frequency ω_p - the frequency where $|G(j\omega)|$ is maximum. Note that you don't have to take any derivatives to find ω_p . Since the numerator is constant, you only have to find where the denominator is minimum.
- Verify that your result in part (b)

$$\omega_p = \frac{1}{\sqrt{LC}}$$

gives the same value gives the same value for ω_p as your graph in Problem (6) for the corresponding values of L and C.

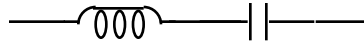- Verify that the impedance of a series LC circuit as follows



is equal to zero at resonance. **Memorize** this result.

- e. Given that the 3dB frequencies of a series RLC circuit are as follows


$$\omega_1 = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \quad \text{and} \quad \omega_2 = +\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

find the **3dB Bandwidth** = $\omega_2 - \omega_1$.

- f. Verify that your result in part (e) gives the same value for the 3dB Bandwidth as your graph in Problem (6) for the corresponding values of L and C.
 g. And finally - express the general equation in part (a) in **standard form** as follows

$$G(j\omega) = \frac{K(j\omega)}{(j\omega)^2 + a(j\omega) + b}$$

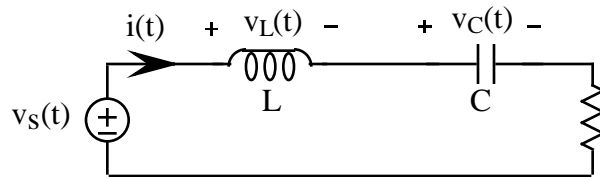8. The objective of this problem is to find the relation between $v_L(t)$ and $v_C(t)$ at resonance in series RLC circuits as follows



- Find $V_L(j\omega)$ and $V_C(j\omega)$ in terms of $I(j\omega)$
- Make use of your result in part (a) to show that $v_L(t)$ and $v_C(t)$ are 180 degrees out of phase.
- Make use of your result in part (b) to sketch $v_L(t)$ and $v_C(t)$ on the same graph at a frequency $\omega < \omega_p$
- Make use of your result in part (b) to sketch $v_L(t)$ and $v_C(t)$ on the same graph at a frequency $\omega = \omega_p$
- Make use of your result in part (b) to sketch $v_L(t)$ and $v_C(t)$ on the same graph at a frequency $\omega > \omega_p$
- Make use of your results in parts (c)-(e) to describe the relationship between $v_L(t)$ and $v_C(t)$ as ω increases from $\omega < \omega_p$ to $\omega > \omega_p$