

ECE 209L - SECOND ORDER CIRCUITS - LAB 13


PARAMETERS OF SECOND ORDER BANDPASS CIRCUITS

FALL 2003

A.P. FELZER

OBJECTIVE

The objective of this lab is to measure and calculate the parameters f_p , f_{BW3dB} and Q_p of second order bandpass circuits like the following

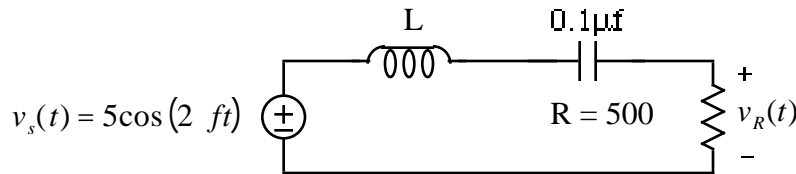

PARTNER 1: L = 10 mh

PARTNER 2: L = 20 mh

LAB

1. **Prelab** - Obtain and measure your resistor and capacitor values. Then compare your nominal and measured values. Put your results in a Table
2. Measure the value of the inductor supplied in the lab
3. Build the circuit and then measure the center frequency f_p and the lower and upper 3dB frequencies f_{L3dB} and f_{U3dB}
4. Make use of your results in Problem (3) to calculate the 3dB bandwidth $f_{BW3dB} = f_{U3dB} - f_{L3dB}$ and $Q_p = \frac{f_p}{f_{BW3dB}}$
5. **Prelab** - Draw the phasor circuit for your measured values (and given L value) and then calculate the transfer function $G(j\omega) = V_R(j\omega)/V_S$
6. **Prelab** - Make use of your equation in Problem (10) to obtain a Mathcad graph of the transfer function $|G(j2\pi f)| = |V_R(j2\pi f)/V_S|$ with f on a log scale
7. **Prelab** - Find f_p , $f_{BW3dB} = f_{U3dB} - f_{L3dB}$ and $Q_p = \frac{f_p}{f_{BW3dB}}$ for your circuit from your graph in Problem (6)
8. Compare your measured and graphical values of f_p , $f_{BW3dB} = f_{U3dB} - f_{L3dB}$ and $Q_p = \frac{f_p}{f_{BW3dB}}$
9. Now remeasure f_p , $f_{BW3dB} = f_{U3dB} - f_{L3dB}$ and $Q_p = \frac{f_p}{f_{BW3dB}}$ in your circuit for a smaller value of R
10. Describe how the smaller value of R affected f_p , f_{BW3dB} and Q_p

11. Sketch $|G(j\omega)| = |V_R(j\omega)/V_S|$ with ω on a log scale for the parameters in Problem (10)
12. How did the change in Q_p affect the shape of the frequency response
13. How in general does the size of Q_p affect the frequency response of a 2nd order bandpass