

ECE 209L - INTRODUCTION TO FILTERS - LAB 16


FIRST ORDER HIGHPASS RC FILTERS

FALL 2003

A.P. FELZER

OBJECTIVE

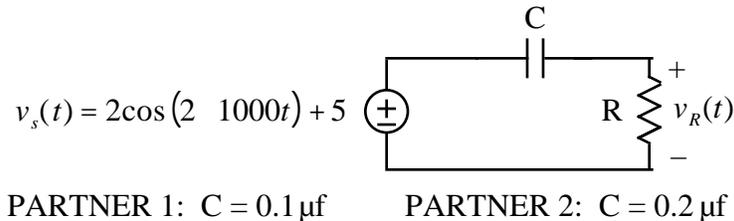The objective of this lab is to make use of superposition to find the steady state response of the following highpass filter.



LAB

1. **Prelab** - Obtain and measure your resistor and capacitor values. Then compare your nominal and measured values. Put your results in a Table
2. **Prelab** - What will happen to $v_R(t)$ in this circuit as R increases. Why
3. **Prelab** - Choose a value for f_{3dB} so that $v_R(t) = 0$. Then make use of your f_{3dB} to sketch a graph of the magnitude of the frequency response $G(j\omega) = V_R(j\omega) / V_S$
4. **Prelab** - Make use of your value of f_{3dB} and the fact that the transfer function of our first order highpass RC circuit is given by $G(j\omega) = \frac{j\omega}{j\omega + f_{3dB}}$ to find $G(j\omega)$
5. **Prelab** - Make use of your transfer function in Problem (4) to find and sketch $v_R(t)$
6. **Prelab** - Make use of the fact that in our circuit $f_{3dB} = \frac{1}{2RC}$ to find R for your f_{3dB} in Problem (3)
7. Build your filter and then make use of a scope to sketch and obtain an equation for $v_R(t)$
8. Compare DC offsets and amplitudes of the sinusoids of your calculated and measured $v_R(t)$'s
9. **Prelab** - Choose a value for f_{3dB} so that $v_C(t) = 2\cos(2000t)$. Then find and sketch a graph of the magnitude of the corresponding transfer function $G(j\omega)$
10. **Prelab** - Make use of your transfer function to calculate and sketch $v_R(t)$ for your filter
11. **Prelab** - Calculate the value of R for your filter
12. Build your filter and then sketch and write an equation for $v_R(t)$
13. Compare your calculated and measured $v_R(t)$'s