

# ECE 209L - FIRST ORDER CIRCUITS - LAB 7

## FREQUENCY RESPONSES OF FIRST ORDER RC CIRCUITS

FALL 2003


A.P. FELZER

### OBJECTIVE

The objective of this lab is to see how the amplitudes of the sinusoidal steady state responses of first order RC circuits vary as a function of frequency

### LAB

1. Given the following circuit

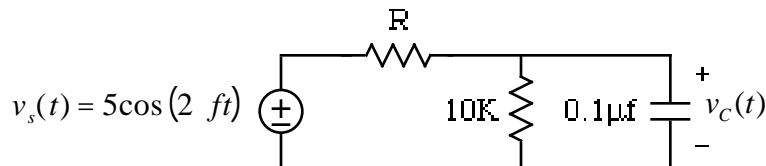


PARTNER 1:  $R = 4.7K$

PARTNER 2:  $R = 10K$

- a. **Prelab** - Obtain and measure your resistor and capacitor values. Then compare your nominal and measured values. Put your results in a Table
- b. Build the circuit and then describe what happens to the magnitude of the sinusoidal steady state voltage  $v_C(t)$  as you increase the frequency of the input  $v_s(t)$ . Illustrate with graphs of  $v_C(t)$
- c. Explain why the amplitude of the sinusoidal steady state response of  $v_C(t)$  behaves the way it does as you increase the frequency

2. Given the following circuit

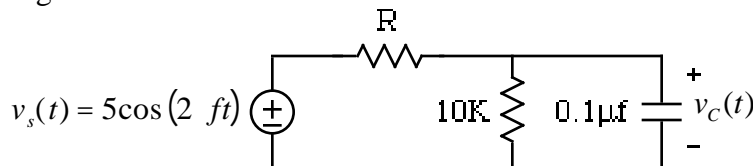

PARTNER 1:  $R = 1K$

PARTNER 2:  $R = 2K$

- a. **Prelab** - Obtain and measure your resistor and capacitor values. Then compare your nominal and measured values. Put your results in a Table
- b. Build the circuit and then measure the amplitude of the sinusoidal steady state response of  $v_C(t)$  at the frequencies  $f = 0, 500 \text{ Hz}, 1\text{KHz}, 2\text{KHz}$  and  $3\text{KHz}$ . Be sure to monitor the amplitude of  $v_s(t)$  every time you take a measurement at a new frequency to make sure it's still 5 volts
- c. Make use of your measured results in part (b) to calculate  $|G(j2f)| = |V_C(j2f)/V_S|$  at the corresponding frequencies. As usual put your results in a Table
- d. **Prelab** - Draw the phasor circuit with your measured values and then analyze it to obtain  $G(j\omega) = V_C(j\omega)/V_S$
- e. Make use of your transfer function from part (d) to calculate  $|G(j2f)|$  at the frequencies in part (b)
- f. Compare your measured and calculated values of  $|G(j2f)|$  in parts (c) and (e)
- g. What causes the amplitude of  $v_s(t)$  to decrease at least some as  $f$  increases