

ECE 204L - LAB 1 - INTROD TO SWITCHING CIRCUITS 1

LAB OBJECTIVE

The objective of this lab is . . .

LAB RESULTS

1. How To Connect LEDs In Circuits
 - a. Circuit diagram

 - b. How to tell which lead of an LED is the anode

 - c. Measured voltage across the LED when it's ON

2. Switching Circuit With One Switch
 - a. Circuit diagram

 - b. Measured truth table

 - c. Measured timing diagram