

**PROBLEMS YOU SHOULD BE ABLE TO DO
BEFORE YOU TAKE ECE 209**

FALL 1995

A.P. FELZER


1. Sketch each of the following for $x \geq 0$

a. $y = \frac{20}{\sqrt{x^2 + 100}}$


b. $y = \frac{2x}{\sqrt{x^2 + 100}}$

c. $y = \tan^{-1}(x)$

2. Given the following circuit

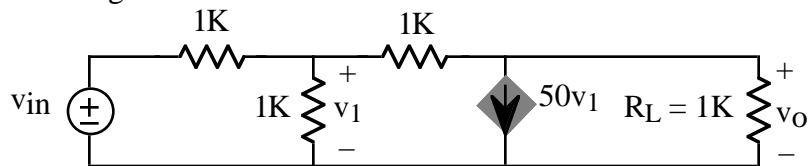


- Write and put in matrix the node equations
 - Solve your equations in part (a) for the node voltages if $v_{in} = 5$ mv
 - Find the power being supplied by the source v_{in} and the power being received by the load R_L if $v_{in} = 5$ mv
 - Find R_{eq} as seen by the source v_{in}
 - Find the transfer function $G = v_o/v_{in}$. Then make use of your result to find v_o if $v_{in} = 5$ volts. Make sure you get the same result as in part (b)
 - Find and draw the Thevenin Equivalent as seen by R_L if $v_{in} = 5$ mv
 - Make use of your Thevenin Equivalent circuit in part (f) to find v_o . Make sure you get the same results as in parts (b) and (e)
 - Make use of SPICE to check your result for v_o when $v_{in} = 5$ mv
3. Given the following circuit with an ideal op amp

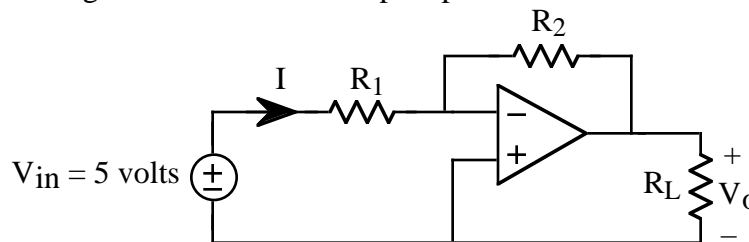

with $R_1 = 1K$, $R_2 = 2K$ and $V_{CC} = 15$ volts


- Find V_o if $V_{in} = 5$ volts
- Find the input resistance $R_{in} = V_{in}/I$
- Sketch $v_o(t)$ if $v_{in}(t) = 10 \cos 100t$
- Find V_- if $V_{in} = 10$ volts

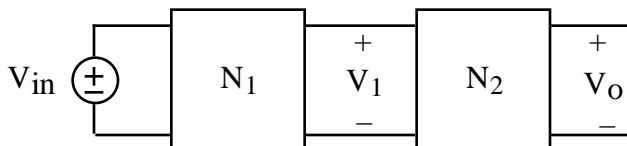4. Under what circumstances does the overall voltage gain $G = V_o/V_{in}$ of the following cascade circuit




equal the product of the open circuit voltage gains of the individual sections. Explain why

5. Given the following circuit

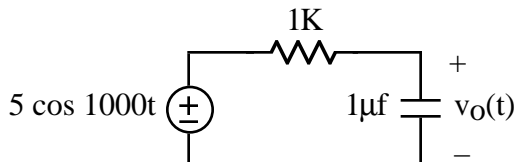

- Find and then sketch the sinusoidal steady state response of $v_o(t)$ by writing and solving the differential equation for the forced response
 - Use a SPICE transient analysis to check your results in part (a). Explain how you were able to determine the phase of the steady state response from the graph
 - How will increasing the frequency of the input affect the magnitude of the sinusoidal steady state $v_o(t)$. Explain why
6. Given the following circuit in the sinusoidal steady state

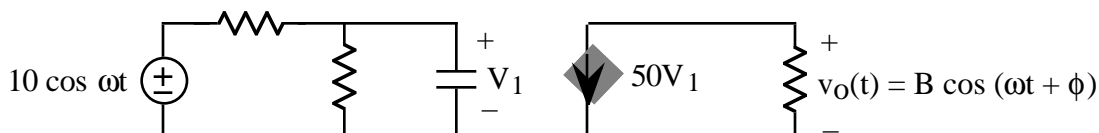

Sketch a graph of the magnitude B of the sinusoidal steady state response as a function of frequency ω . Describe your curve. Explain why it looks the way it does

7. Repeat Problem (5) for $i(t)$ in the following RL circuit

