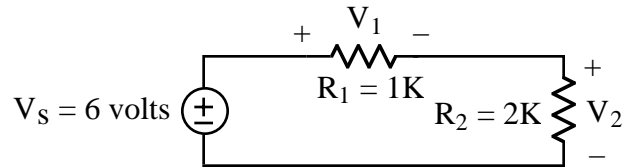


## EXAMPLES OF TABLES

FALL 1998

A.P. FELZER

Here are two examples illustrating how to make Tables for the following circuit.



Note in particular that each Table has a **conclusion**

### 1. Measuring Of Resistor Values

RESISTOR	NOMINAL VALUE	MEASURED VALUE	% DIFF
$R_1$	1K	1K	0
$R_2$	2K	2.05K	0.25%

$R_1$  and  $R_2$  are both within 5% tolerance

### 2. Comparing Calculated and Measured Voltages

VOLTAGE	CALCULATED VALUE	MEASURED VALUE	% DIFF
$V_1$	2 v	2.1 v	5%
$V_2$	4 v	3.9 v	2.5%

The measured voltages are reasonably close to the calculated values